

CS10720 Problems and Solutions

Thomas Jansen

Today: Boolean Logic, Truth Tables
and Digital Circuits

February 11th

Announcements

Remember **deadline** for portfolio submission **Friday, 7pm**
containing **lecture summary** only for today
and **answers to both** questions for one practicals problem

Announcement **no** feedback on Monday
but **later** next week (and I don't know yet when)


But why?

Fact marking and feedback takes about 7 minutes per student
adding up to about 18 hours

But that's what a lecturer's weekend is for!

Well... normally that's what I do but this weekend...

Saturday

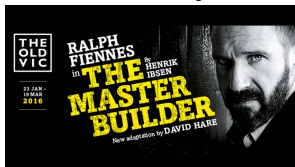

Sunday



Plans for Today

① Boolean Logic

Introduction

Computing with Boolean Logic

② Hardware

Logical Gates

Building and Reading Digital Circuits

③ Summary

Summary & Take Home Message

A Tiny Bit of Logic and Algebra...

Propositional logic

- **proposition** is a statement that is either **true** or **false** (Remark **independent** of whether you know)
- two propositions can be combined using the operators **and** and **or** to form a new one
 - when using **and**, new proposition true if both propositions true
 - when using **or**, new proposition true if at least one of the propositions true
- using **not** new proposition can be formed using one proposition
new proposition is true if old proposition is false

Definition by **truth tables** for propositions A , B

and (conjunction)			or (disjunction)			not (negation)	
A	B	A and B	A	B	A or B	A	not A
false	false	false	false	false	false	false	true
false	true	false	false	true	true	true	false
true	false	false	true	false	true		
true	true	true	true	true	true		

Boolean Algebra

Definition

Let $B = \{0, 1\}$. For $x, y \in B$, let $x \cap y = \min\{x, y\}$. For $x, y \in B$, let $x \cup y = \max\{x, y\}$. For $x \in B$, let $\bar{x} = 1 - x$. $(B, \cup, \cap, -)$ is called **Boolean algebra**.

Observe

x	y	$x \cap y$	x	y	$x \cup y$	x	\bar{x}
0	0	0	0	0	0	0	1
0	1	0	0	1	1	1	0
1	0	0	1	0	1		
1	1	1	1	1	1		

Observe **close relationship** between
propositional logic and **Boolean algebra**

Notation


we use interchangeably

'true' and '1', 'false' and '0'

' x and y ', ' $x \cap y$ ', ' $x \wedge y$ ', ' $x \cdot y$ ', ' xy '

' x or y ', ' $x \cup y$ ', ' $x \vee y$ '

George Boole (1815–1864)

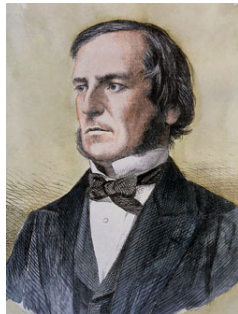

More Operations

Conjunction (and) Disjunction (or) Negation (not)

x	y	$x \wedge y$	x	y	$x \vee y$	x	\bar{x}
0	0	0	0	0	0	0	1
0	1	0	0	1	1	1	0
1	0	0	1	0	1		
1	1	1	1	1	1		

Implication (if) Equivalence (iff)

x	y	$x \Rightarrow y$	x	y	$x \Leftrightarrow y$
0	0	1	0	0	1
0	1	1	0	1	0
1	0	0	1	0	0
1	1	1	1	1	1

Exclusive Or (xor) NAND (not and)

x	y	$x \oplus y$	x	y	$\overline{x \wedge y}$
0	0	0	0	0	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	0	1	1	0

‘Computing’ with Boolean Logic

- commutativity

$$(x \vee y) = (y \vee x) \text{ (also for } \wedge, \oplus, \Leftrightarrow)$$

- associativity

$$((x \wedge y) \wedge z) = (x \wedge (y \wedge z)) \text{ (also for } \vee, \oplus, \Leftrightarrow)$$

- distributivity

$$(x \vee (y \wedge z)) = ((x \vee y) \wedge (x \vee z))$$

$$(x \wedge (y \vee z)) = ((x \wedge y) \vee (x \wedge z))$$

- elimination of double negation

$$(\neg(\neg x)) = x$$

- De Morgan

$$(\overline{x \wedge y}) = (\bar{x} \vee \bar{y}), (\overline{x \vee y}) = (\bar{x} \wedge \bar{y})$$

- elimination of implication

$$(x \Rightarrow y) = (\bar{x} \vee y)$$

- elimination of equivalence

$$(x \Leftrightarrow y) = ((x \Rightarrow y) \wedge (y \Rightarrow x))$$

Proofs by truth tables (i. e., complete enumeration)

One Example Proof: De Morgan

(well, two actually. . .)

x	y	$\overline{x \wedge y}$	$\overline{x} \vee \overline{y}$	equal?
0	0	1	1	✓
0	1	1	1	✓
1	0	1	1	✓
1	1	0	0	✓

proves $(\overline{x \wedge y}) = (\overline{x} \vee \overline{y})$

x	y	$\overline{x \vee y}$	$\overline{x} \wedge \overline{y}$	equal?
0	0	1	1	✓
0	1	0	0	✓
1	0	0	0	✓
1	1	0	0	✓

proves $(\overline{x \vee y}) = (\overline{x} \wedge \overline{y})$

Boolean Functions

Definition function $f: B^n \rightarrow B$ (Remember $f: \{0,1\}^n \rightarrow \{0,1\}$) is called **Boolean function** over n variables

Example $f: B^3 \rightarrow B$

x	y	z	$f(x,y,z)$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Truth table **bulky**. Are there more compact representations?

Observation if we **agree on order** then **value vector** suffices
 $(0, 1, 0, 0, 0, 1, 0, 1)$

Can we find a Boolean expression for this?

Minterms

Definition conjunction of all n variables (either negated or unnegated) is called **minterm** for these n variables

Example

minterm $x \bar{y} z$			
x	y	z	$x \bar{y} z$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

Observation minterm 1 for exactly one input
and 0 everywhere else
holds for every minterm

Consequence using disjunction of minterms
any Boolean function can be easily represented

Disjunctive Normal Forms

Remember example $f: B^3 \rightarrow B$

x	y	z	$f(x, y, z)$	$\bar{x} \bar{y} z$	$x \bar{y} z$	$x y z$
0	0	0	0	0	0	0
0	0	1	1	1	0	0
0	1	0	0	0	0	0
0	1	1	0	0	0	0
1	0	0	0	0	0	0
1	0	1	1	0	1	0
1	1	0	0	0	0	0
1	1	1	1	0	0	1

Consequence $f(x, y, z) = (\bar{x} \bar{y} z) \vee (x \bar{y} z) \vee (x y z)$

Definition representation of Boolean function f
by disjunction of minterms
is called **disjunctive normal form**

Truth Tables for Boolean Functions


How can we compute a truth table for a complex Boolean function like $f(w, x, y, z) = (w \vee x) \oplus ((w \wedge y) \vee (w \wedge (\overline{x \vee z})))$?

Idea construct truth table sub-expression by sub-expression


w	x	y	z	t_1 $w \vee x$	t_2 $w \wedge y$	t_3 $\overline{x \vee z}$	t_4 $w \wedge t_3$	t_5 $t_2 \vee t_4$	f $t_1 \oplus t_5$	$f(w, x, y, z)$
0	0	0	0	0	0	1	0	0	0	0
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0	0	0	0
0	0	1	1	0	0	0	0	0	0	0
0	1	0	0	1	0	0	0	0	1	1
0	1	0	1	1	0	0	0	0	1	1
0	1	1	0	1	0	0	0	0	1	1
0	1	1	1	1	0	0	0	0	1	1
1	0	0	0	1	0	1	1	1	0	0
1	0	0	1	1	0	0	0	0	1	1
1	0	1	0	1	1	1	1	1	0	0
1	0	1	1	1	1	0	0	1	0	0
1	1	0	0	1	0	0	0	0	1	1
1	1	0	1	1	0	0	0	0	1	1
1	1	1	0	1	1	0	0	1	0	0
1	1	1	1	1	1	0	0	1	0	0

Logical Gates and Circuits


negation

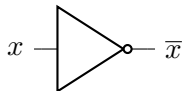


conjunction

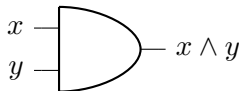


disjunction

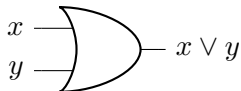

exclusive or (XOR)

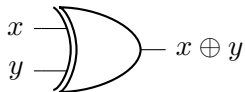


NAND

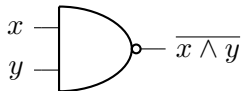

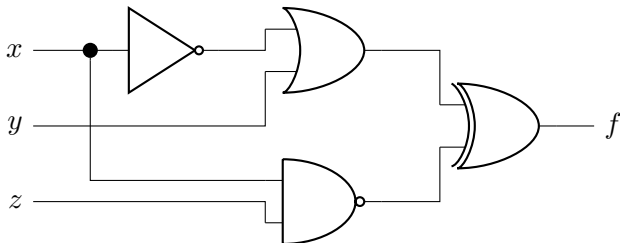Example: Building a Simple Digital Circuit


$$f(x, y, z) = (\bar{x} \vee y) \oplus \overline{x \wedge z}$$



Remark with 'simple' we mean 'no loops'
(i. e., no paths from an output of a gate to its own input)

Remark better idea of such circuits by 'playing' with Logisim
<http://www.cburch.com/logisim/>
freely available as .jar file
and in custom versions for Mac and Windows

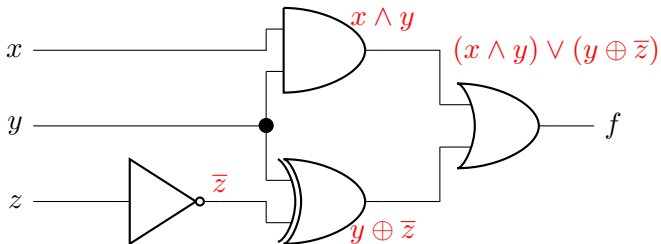Example: Reading a Simple Digital Circuit



$$f(x, y, z) = (x \wedge y) \vee (y \oplus \bar{z})$$

Summary & Take Home Message

Things to remember

- propositional logic and Boolean algebra
- Boolean operators
- truth tables
- digital gates and digital circuits

Take Home Message

- Boolean algebra is fundamental for computers, in particular computer hardware.
- Computations with Boolean algebra are tedious, not difficult.

Lecture feedback <http://onlinetted.com>